



VLSI LAB
CODE: CSE-406
Experiment No:
5

Submission Date:10.10.2020

Submitted By:
Natasha Tanzila
Class Roll: 2220
Semester: 4.1
Dept. of CSE,JU.

.....

Submitted To:
1.Dr. Abu Sayed Md.
Mostafizur Rahaman,
Professor,
2.Anup Majumder,
Lecturer,
Dept. of CSE,JU.

Experiment No: 5

Experiment Name: Verification of nMOS and pMOS DC characteristics.

Objectives:

- ① To find the MOS model parameters for the transistors and then by "paper and pencil" manually calculate the DC characteristics of I_{DS} current vs V_{DS} voltage, using simple current equations for MOS model level 1 to determine a number of corresponding value pairs of $(I_{DS}; V_{DS})$ with gate-source voltage V_{GS} a constant $> V_{th}$.
- ② Use circuit simulator of Microsim to do a DC simulation of the I_{DS} current vs V_{DS} voltage and the result of the two methods compared.
- ③ Calculation of the threshold voltage.

NMOS

Theory:

There are 3 regions and for calculation of the value I_{DS} . The nMOS transistor I_{DS} current versus V_{DS} voltage equations are stated below for level 1 stimulation and other calculations.

- ☐ Cut-off mode: $I_{DS} = 0$ when $V_{GS} < 0$
- ☐ Triod/Linear Region: $I_{DS} = k_n \{ (V_{GS} - V_{th}) V_{DS} - \frac{1}{2} V_{DS}^2 \}$
when, $V_{DS} < V_{GS} - V_{th} \dots (1)$
- ☐ Saturation region: $I_{DS} = \frac{1}{2} k_n \{ (V_{GS} - V_{th})^2 (1 + \lambda V_{DS}) \}$
when, $V_{DS} > V_{GS} - V_{th} \dots (2)$

Procedure:

a) Level 1 MOS model equations to calculate DC values for the drain current I_{DS} vs drain-source voltage V_{DS} (paper & pencil)

Values $V_{GS} = +2.0V$ is taken. for the following values of $V_{DS} = 0.5V, 1.0V, 1.5V, 2.0V, 2.5V$ and to determine the region $V_{DS} - (V_{GS} - V_{th})$ is calculated then whatever the region it follows either cut off or (1) or (2) equation must be followed. Here we should consider $V_{th} = 0.45V$, $\mu_0 = \mu_n = 0.06$, $r = 0.4$.

Calculations:

$$(i) V_{DS} - (V_{GS} - V_{th}) < 0$$

$$\Rightarrow 0.5 - (2 - 0.45) < 0$$

$\Rightarrow -1.05 < 0$; it satisfies the linear region.

$$I_{DS} = k_n \left\{ (V_{GS} - V_{th}) V_{DS} - \frac{1}{2} V_{DS}^2 \right\}$$

$$= 8.424 \times 10^{-4} \left[(2 - 0.45) \times 0.5 - \frac{1}{2} \times (0.5)^2 \right]$$

$$= 8.424 \times 10^{-4} \times 0.65$$

$$= 5.4756 \times 10^{-4} A$$

$$= 5.4756 \times 10^{-4} \times 10^6 \mu A$$

$$= 547.56 \mu A$$

$$k_n = k'_n \left(\frac{W_n}{L_n} \right)$$

$$= k'_n \times 2$$

$$k'_n = \mu_n \times C_{ox}$$

$$\mu_n = 0.60 m^2/V\text{-sec}$$

$$C_{ox} = \epsilon_{ox} / t_{ox} = 7.02 \times 10^{-3}$$

$$\epsilon_{ox} = 3.51 \times 10^{-14} [F/m]$$

$$t_{ox} = 5.000 nm = 5 \times 10^{-9} m$$

$$k_n = 0.060 \times 7.02 \times 10^3 = 4.212 \times 10^{-4}$$

$$\begin{aligned}
 \text{(ii)} \quad V_{DS} - (V_{GS} - V_{TH}) &< 0 \\
 &= 1 - (2 - 0.45) < 0 \\
 &= -0.55 < 0 ; \text{ it satisfies linear region.}
 \end{aligned}$$

$$\begin{aligned}
 I_{DS} &= K_n \left\{ (V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right\} \\
 &= 8.424 \times 10^{-4} \left[(2 - 0.45) \times 1 - \frac{1}{2} (1)^2 \right] \\
 &= 8.424 \times 10^{-4} \times 1.05 \\
 &= 8.8452 \times 10^{-4} \text{ A} \\
 &= 8.8452 \times 10^{-4} \times 10^6 \mu\text{A} \\
 &= 884.52 \mu\text{A}
 \end{aligned}$$

$$\begin{aligned}
 \text{(iii)} \quad V_{DS} - (V_{GS} - V_{TH}) &< 0 \\
 \Rightarrow 1.5 - (2 - 0.45) &< 0 \\
 \Rightarrow -0.05 < 0 ; \text{ it satisfies linear region.}
 \end{aligned}$$

$$\begin{aligned}
 I_{DS} &= K_n \left\{ (V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right\} \\
 &= 8.424 \times 10^{-4} \left\{ (2 - 0.45) \times 1.5 - \frac{1}{2} (1.5)^2 \right\} \\
 &= 8.424 \times 10^{-4} \times 1.2 \\
 &= 1.01088 \times 10^{-3} \text{ A} \\
 &= 1.01088 \times 10^{-3} \times 10^6 \mu\text{A} \\
 &= 1010.88 \mu\text{A}
 \end{aligned}$$

$$\begin{aligned}
 \text{(iv)} \quad V_{DS} - (V_{GS} - V_{TH}) &> 0 \\
 \Rightarrow 2 - (2 - 0.45) &> 0 \\
 \Rightarrow 0.45 > 0 ; \text{ it satisfies saturation region.} \\
 I_{DS} &= \frac{1}{2} K_n (V_{GS} - V_{TH})^2 \\
 &= \frac{1}{2} \times 8.424 \times 10^{-4} (2 - 0.45)^2 \\
 &= \frac{1}{2} \times 8.424 \times 10^{-4} \times 2.4025 \\
 &= 1.011933 \times 10^{-3} \text{ A} = 1011.933 \mu\text{A}
 \end{aligned}$$

$$\begin{aligned}
 v) V_{DS} - (V_{GS} - V_{th}) &> 0 \\
 \Rightarrow 2.5 - (2 - 0.45) &> 0 \\
 \Rightarrow 0.95 > 0; \text{ it satisfies saturation region} \\
 I_{DS} &= \frac{1}{2} K_n \{ (V_{GS} - V_{th})^2 \} \\
 &= \frac{1}{2} \times 8.424 \times 10^{-4} \times (2 - 0.45)^2 \\
 &= 1.011933 \times 10^{-3} \text{ A} \\
 &= 1011.933 \mu\text{A}
 \end{aligned}$$

Table of values: $V_{GS} = +2.0\text{V}$ and $k_n/L_n = 2$

| $V_{DS} (\text{V})$ | 0.5 | 1.0 | 1.5 | 2.0 | 2.5 |
|--|--------|--------|---------|------------|------------|
| $V_{DS} - (V_{GS} - V_{th})$ | -1.05 | -0.55 | -0.05 | 0.45 | 0.95 |
| | (1) | (1) | (1) | (2) | (3) |
| | Linear | Linear | Linear | Saturation | Saturation |
| Manual Calculation, $I_{DS} (\mu\text{A})$ | 547.56 | 884.52 | 1010.88 | 1011.933 | 1011.933 |

Excel Calculations & Plotting:

after plotting we will see the graph to be compared further.

WPS Office | nmos.xlsx | pmos.xlsx

Menu | Home | Insert | Page Layout | Formulas | Data | Review | View | Tools | QCL...


Paste | Cut | Copy | Format Painter | Calibri | 11 | A+ | A- | Bold | Italic | Underline | Text Color | Fill Color | Merge and Center | Wrap Text | General | Conditional Formatting | Format as Table | AutoSum | AutoFilter | Sort | Format | Fill | Rows and Columns

L14 | fx

| | A | B | C | D | E | F | G | H | I | J | K | L | M | N |
|---|-------------------------|---|--------|--------|---------|----------|----------|---|---|---|---|---|---|---|
| 1 | VDS | 0 | 0.5 | 1 | 1.5 | 2 | 2.5 | | | | | | | |
| 2 | Manual calculation, IDS | 0 | 547.56 | 884.52 | 1010.88 | 1011.933 | 1011.933 | | | | | | | |
| 3 | | | | | | | | | | | | | | |

PivotTable | Field List | Drag fields onto PivotTable area

In picture, excel table for nmos.

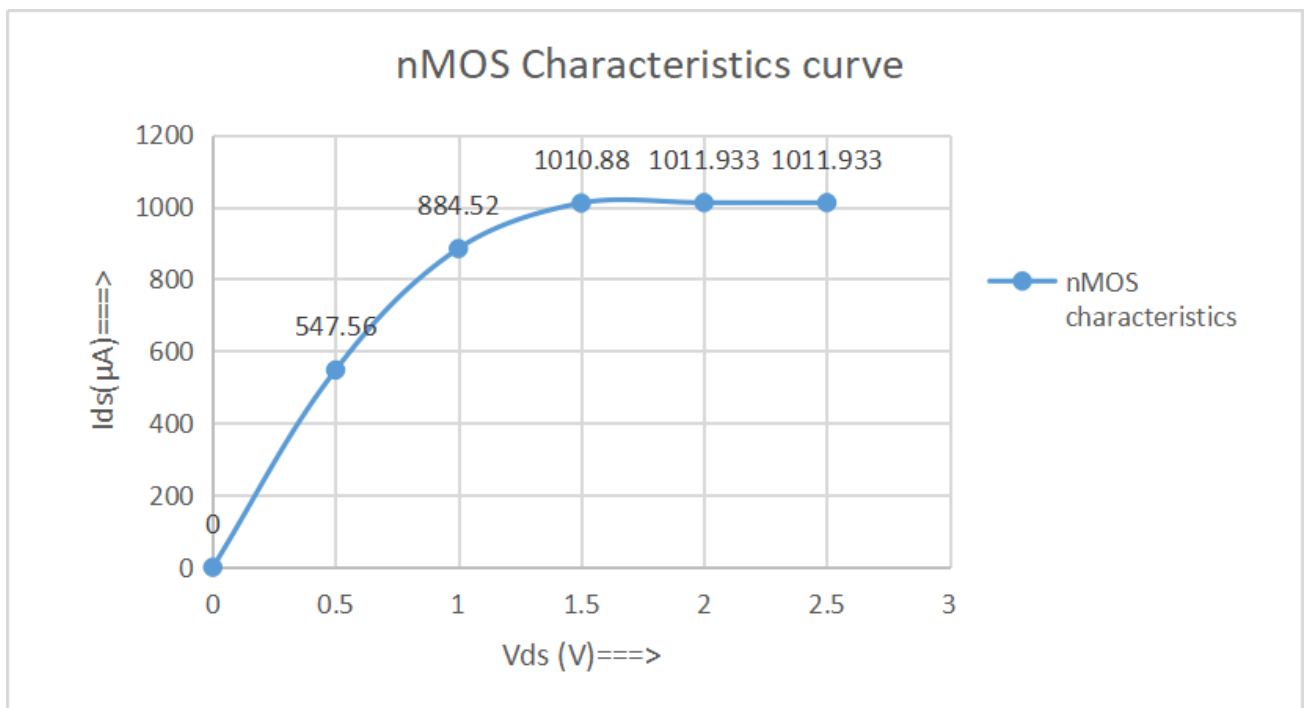

b) Use of "Simulate > MOS characteristic" to generate the DC characteristics I_{DS} for the NMOS transistor in microwind.

After selecting the foundry \rightarrow cmos025.rul
 • Use level1 MOS transistor model.



We will take width & length ratio 48×25 .

Simulate \rightarrow MOS characteristics and then point to the NMOS transistor. Here, choose $V_{DS} = 2.0V$
 then $V_{GS} =$ upto 2.50 and step 0.5. Then click on the draw button.

From Microwind:

| V_{DS} (V) | 0.5 | 1.0 | 1.5 | 2.0 | 2.5 |
|-------------------------------------|--------|--------|---------|----------|---------|
| Manual Calculation I_{DS} (uA) | 547.56 | 884.52 | 1010.88 | 1011.933 | 1011.93 |

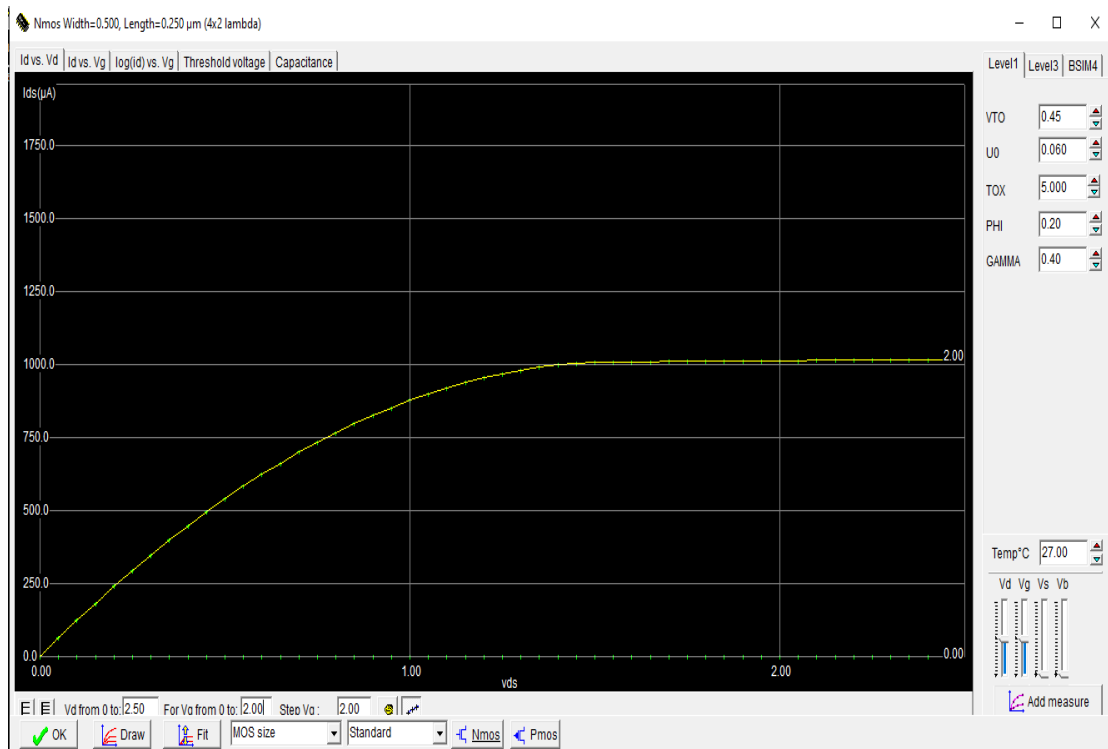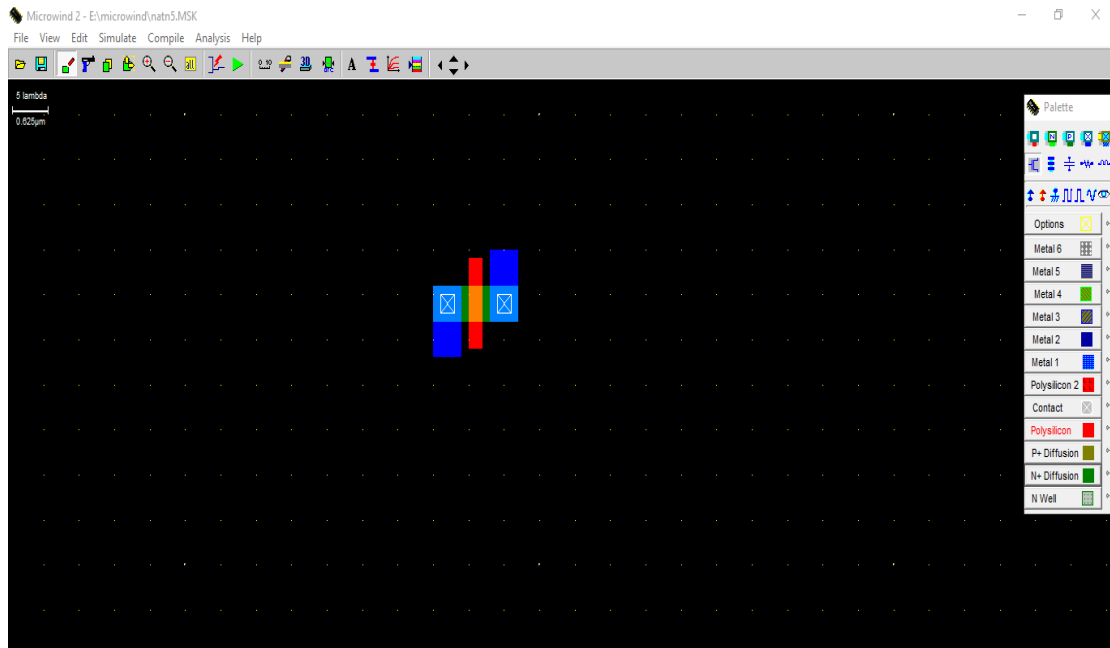We compared, the microwind and pen-pencil I_{DS} and then we ought for the calculation of threshold voltage factor.



c) Calculation of the threshold voltage factor (γ)

We have considered that the threshold voltage factor $\gamma = 0$. We have found that

$$U_{TD} = 0.45V.$$

Result: The lab objectives are successfully observed and verified with theoretical calculation.

PMOS

Theory: The following regions will be used for the calculations. The regions are 3 as follows.

cut-off region: $V_{gs} < V_t$, $I_{ds} = 0$

Linear Region: $V_{gs} < V_t$ and

$$V_{ds} > V_{gs} - V_t$$

$$I_{ds} = -k_p [(V_{gs} - V_t)V_{ds}^{1/2} (V_{ds})^2]$$

Saturation Region: $V_{ds} < V_{gs} - V_t$

$$I_{ds} = -k_p/2 (V_{gs} - V_t)^2$$

Procedure:
a) Level 1 MOS model equations to calculate DC values for the I_{ds} .
We will first calculate the values of I_{ds} manually by paper & pencil method. Then we will plot it in excel for further calculations & comparisons.

$$\begin{aligned}
 \text{(i)} \quad & V_{ds} = 0.5 \\
 & V_{ds} - (V_{gs} - V_t) < 0 \\
 \Rightarrow & 0.5 - (2 + 0.45) < 0 \\
 \Rightarrow & 0.5 - 2.45 < 0 \\
 \Rightarrow & -1.95 < 0 ; \text{ it satisfies saturation region}
 \end{aligned}$$

$$\begin{aligned}
 I_{ds} &= -K_p/2 (V_{gs} - V_t)^2 \\
 &= -\frac{1}{2} \times 8.424 \times 10^{-4} (2 + 0.45)^2 \\
 &= -2.528253 \times 10^{-3} \text{ A} \\
 &= -2528.253 \mu\text{A}
 \end{aligned}
 \quad \left| \quad \begin{aligned}
 K_p &= \mu_p C_{ox} \frac{W}{L} \\
 &= 0.06 \times \frac{3.9 \times 10^{-11}}{5 \times 10^{-9}} \times 2 \\
 &= 8.424 \times 10^{-4}
 \end{aligned}$$

$$\begin{aligned}
 \text{(ii)} \quad & V_{ds} = 1 < 0 \\
 & V_{ds} - (V_{gs} - V_t) < 0 \\
 \Rightarrow & 1 - (2 + 0.45) < 0 \\
 \Rightarrow & 1 - 2.45 < 0 \\
 \Rightarrow & -1.45 ; \text{ it satisfies saturation region.}
 \end{aligned}$$

$$\begin{aligned}
 I_{ds} &= -\beta/2 (V_{gs} - V_t)^2 \\
 &= -\frac{1}{2} \times 8.424 \times 10^{-4} (2 + 0.45)^2 \\
 &= -2528.253 \mu\text{A}
 \end{aligned}$$

$$(iii) V_{ds} = 1.5$$

$$V_{ds} - (V_{gs} - V_t) < 0$$

$$\Rightarrow 1.5 - (2 + 0.45) < 0$$

$$\Rightarrow 1.5 - 2.45 < 0$$

$\Rightarrow -0.95 < 0$; it satisfies the saturation region

$$I_{ds} = -\frac{1}{2} K_p (V_{gs} - V_t)^2$$

$$= -\frac{1}{2} \times 8.424 \times 10^{-4} (2 + 0.45)^2$$

$$= -2528.253 \mu A$$

$$iv) V_{ds} = 2$$

$$V_{ds} - (V_{gs} - V_t) < 0$$

$$\Rightarrow 2.5 - (2 + 0.45) < 0$$

$$\Rightarrow 2.5 - 2.45 < 0$$

$\Rightarrow 0.05$; it satisfies saturation region

$$I_{ds} = -\frac{1}{2} K_p (V_{gs} - V_t)^2$$

$$= -\frac{1}{2} \times 8.424 \times 10^{-4} (2 + 0.45)^2$$

$$= -2528.253 \mu A$$

$$v) V_{ds} = 2.5$$

$$V_{ds} - (V_{gs} - V_t) > 0$$

$$\Rightarrow 2.5 - (2 + 0.45) > 0$$

$$\Rightarrow 2.5 - 2.45 > 0$$

$\Rightarrow 0.05$; it satisfies the linear region.

$$I_{ds} = -K_p \left[(V_{gs} - V_t) V_{ds} - \frac{1}{2} V_{ds}^2 \right]$$

$$= -8.424 \times 10^{-4} \left[(2 + 0.45) \times 2.5 - \frac{1}{2} (2.5)^2 \right]$$

$$= -8.424 \times 10^{-4} \times 3$$

$$= -2.5272 \times 10^{-3} A$$

$$= -2527.2 \mu A$$

for the values of these we can put it in this table:

| $V_{ds} (V)$ | 0.5 | 1.0 | 1.5 | 2.0 | 2.5 |
|------------------------------|------------------------|------------------------|-----------------------|-----------------------|----------------------|
| $V_{ds} - (V_{gs} - V_{tp})$ | -1.95 | -1.45 | -0.95 | 0.45 | 0.05 |
| | saturation | saturation | saturation | saturation | Linear |
| Manual calculation | | | | | |
| $I_{ps} (\mu A)$ | -2528. 2532 μA | -2528. 2532 μA | -2528. 253 μA | -2528. 253 μA | -2527.2 2 μA |

WPS Office | nmos.xlsx | pmos.xlsx


Menu | Home | Insert | Page Layout | Formulas | Data | Review | View | Tools | QCL...

Paste | Cut | Copy | Format Painter | Calibri | 11 | A+ | A- | Bold | Italic | Underline | Text Color | Fill Color | Merge and Center | Wrap Text | General | Conditional Formatting | Format as Table | AutoSum | AutoFilter | Sort | Format | Fill | Rows and Columns

M16 | fx

| | A | B | C | D | E | F | G | H | I | J | K | L | M |
|---|----------------------------|---|----------|----------|----------|----------|--------|---|---|---|---|---|---|
| 1 | Vds | 0 | 0.5 | 1 | 1.5 | 2 | 2.5 | | | | | | |
| 2 | Manual calculation Ids(μA) | 0 | 2528.253 | 2528.253 | 2528.253 | 2528.253 | 2527.2 | | | | | | |
| 3 | | | | | | | | | | | | | |

PivotTable | Field List | Drag fields onto PivotTable area

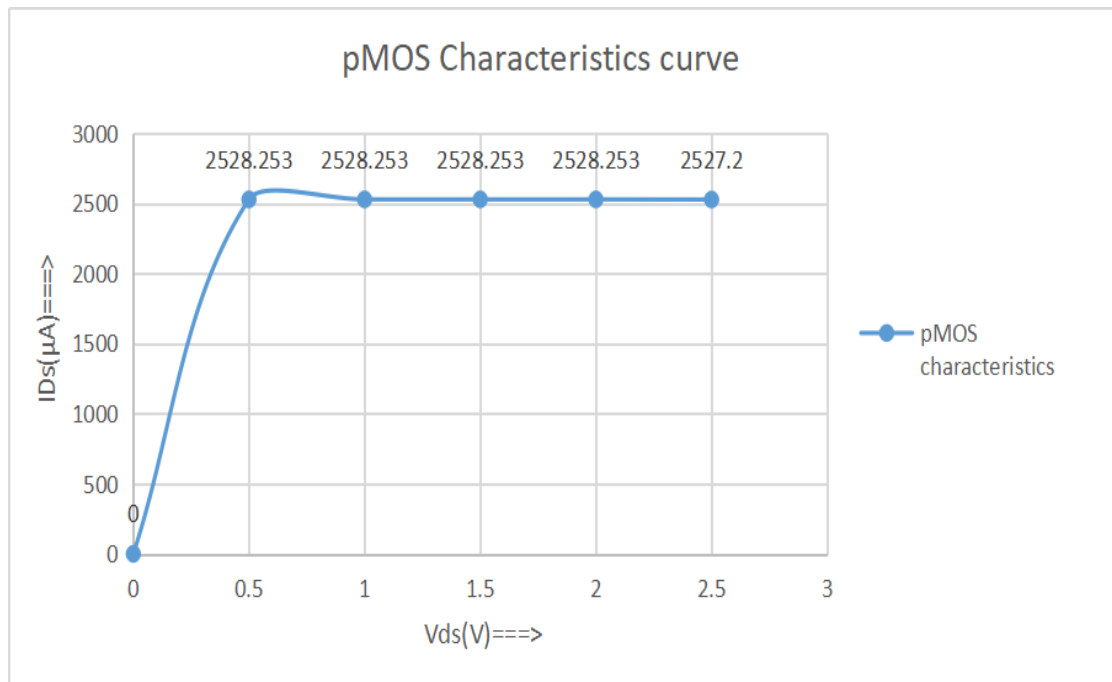


b) Use of "simulate > MOS characteristics" to generate the DC characteristics I_{DQ} vs V_{DS} for the PMOS transistor in microwind.

☑ Selecting the foundry → CMOS 0.25.oul
- Using level1 MOS transistor Model.


☑ Now generating nMOS transistor of width and length ratio is 4×20 from palette.

☑ Now clicking simulate → MOS characteristics.

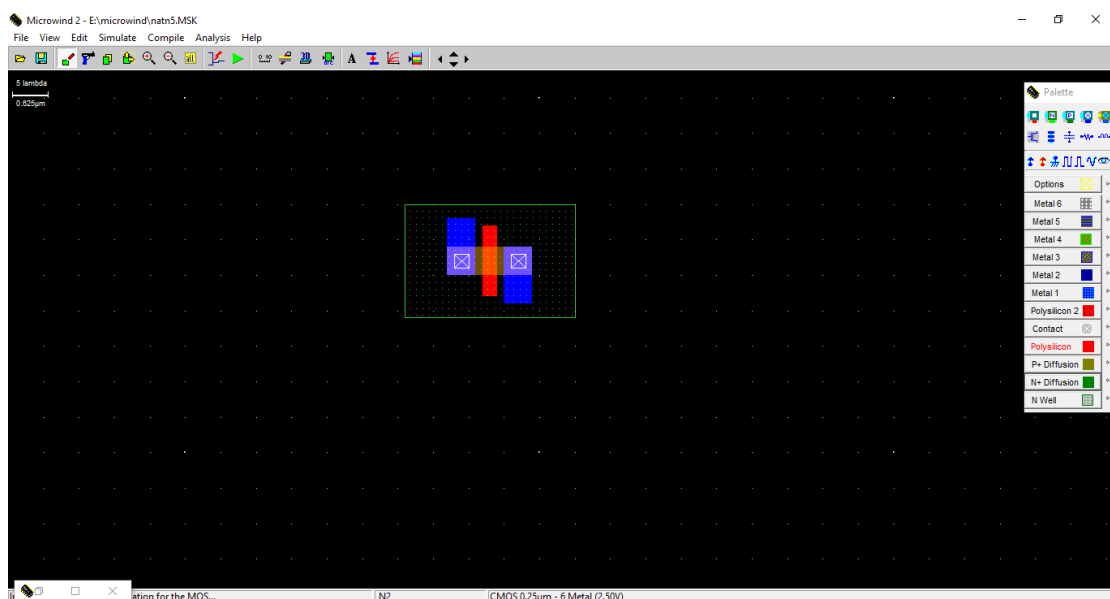☑ Now steps should be 2.0 and others accordingly.



In picture, PMOS transistor.

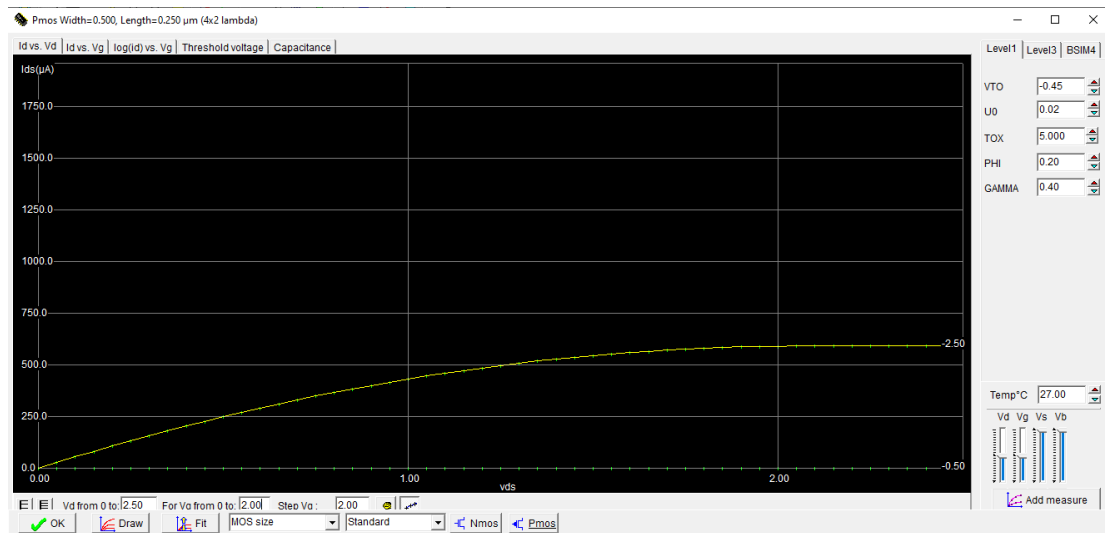

Result:

The lab objectives are successfully observed and verified with theoretical calculation.