REPORT

on

"VLSI Circuits Design Laboratory"

Experiment-III: "Implementing CMOS-NAND & CMOS-NOR using Microwind 2."
Course Code: CSE-406

Submitted by

Md. Tazel Hossan
Roll No. 1921 of 2017-18
4th Year 1st Semester

Submitted to

Anup Majumder
Lecturer

Department of Computer Science & Engineering
Jahangirnagar University
Savar-1342

Date Of Submission:25 Jun, 2022